

ELECTRONIC CIRCUITS

MINI PROJECT (IC741)

Name	ID
Abdullah Abdulqader Elyas	445801983
Meshal Nasser Alsalem	445802089
Faisal Sultan Asiri	444809886
Meshal Zaid Ali Asiri	444809885



INTRODUCTION

This project demonstrates a simple temperature-activated circuit using an Op-Amp 741, a thermistor, and a trimpot.

The goal:

The circuit is to turn ON a lamp when the temperature near the thermistor increases, such as when a flame or heat source is brought close.


A series of three parallel white diagonal lines extending from the bottom right towards the top right of the slide.

Requirements:


1- IC471




2- perbord

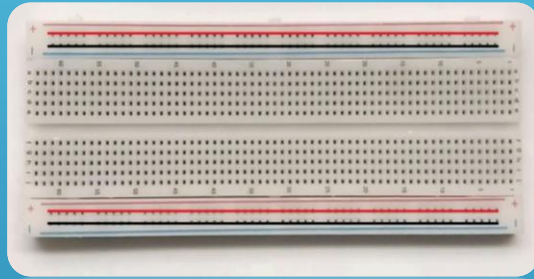

3- Resistors

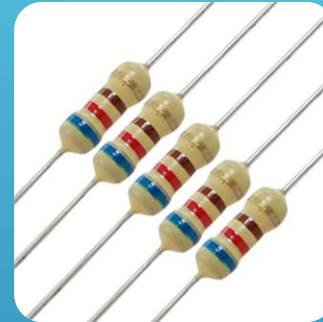

4- potentiometer terminal

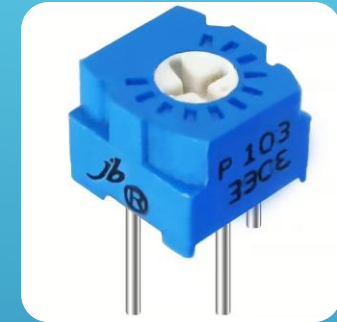

5- Thermal resistance



6-Wires



CIRCUIT DESCRIPTION

The circuit contains three important components:

1.Thermistor (NTC):


Its resistance decreases when temperature increases. This change in resistance creates a change in voltage.

2.Trimpot (Variable Resistor):


Used to set a reference voltage for the Op-Amp. This reference determines the temperature level at which the lamp will turn ON.

3.Op-Amp 741 (Comparator Mode):


The 741 compares the thermistor voltage with the reference voltage set by the trimpot.

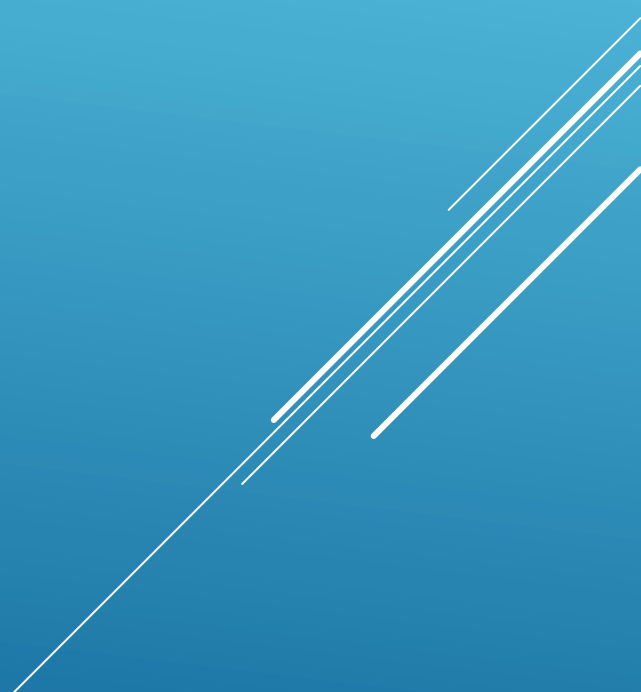A series of three parallel white diagonal lines on the right side of the slide, pointing upwards and to the right.

WORKING PRINCIPLE

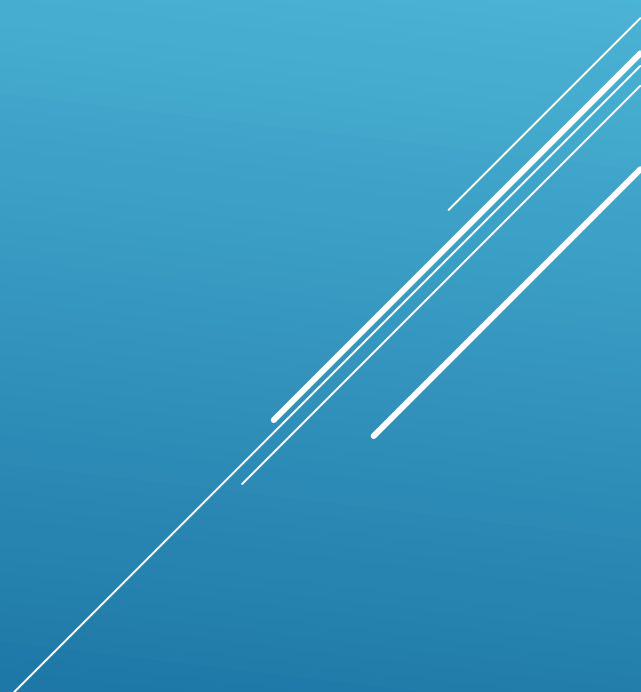- The heat source (such as a lighter or candle) moves closer to the thermistor, the thermistor's resistance drops.
 - This produces a voltage that crosses the reference set by the trimpot.
 - At this point, the 741 output deactivates the lamp, indicating that the temperature threshold has been reached.
- 
- A series of three parallel white diagonal lines are positioned in the bottom right corner of the slide, extending from the middle of the right edge towards the bottom left.

CIRCLE DRAWING

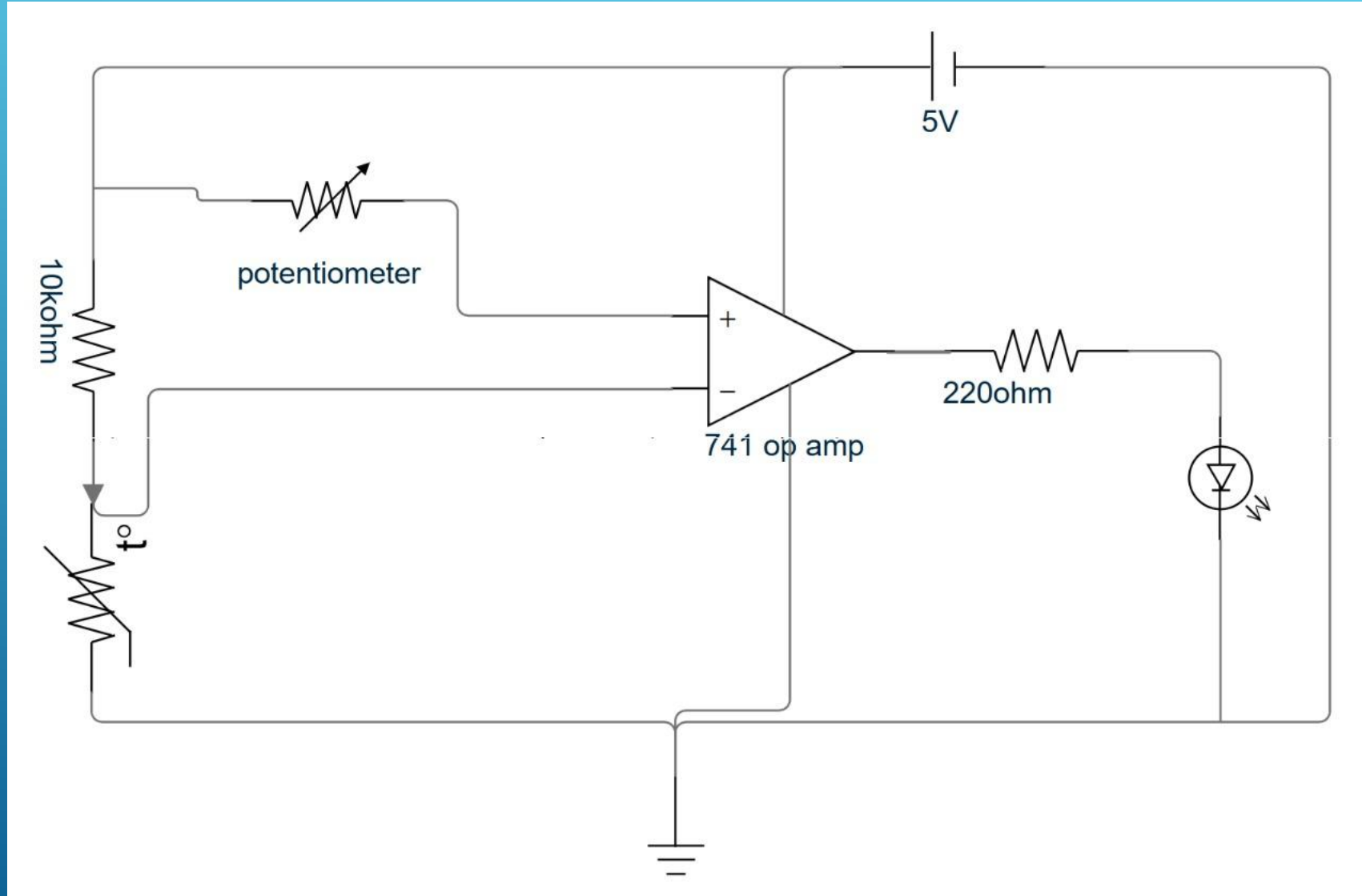

WHY DID WE USE IT IC741?


We used the IC 741 because it can detect small voltage changes from the thermistor, amplify them, and reliably control the lamp when the temperature rises.

Its simplicity and availability make it ideal for this experiment.

Several thin, white, parallel diagonal lines are positioned on the right side of the slide, extending from the middle towards the bottom right corner.

USES

You can use this simple project as an early fire-detection indicator, where the LED turns off when heat is detected, helping alert you to potential fire hazards.

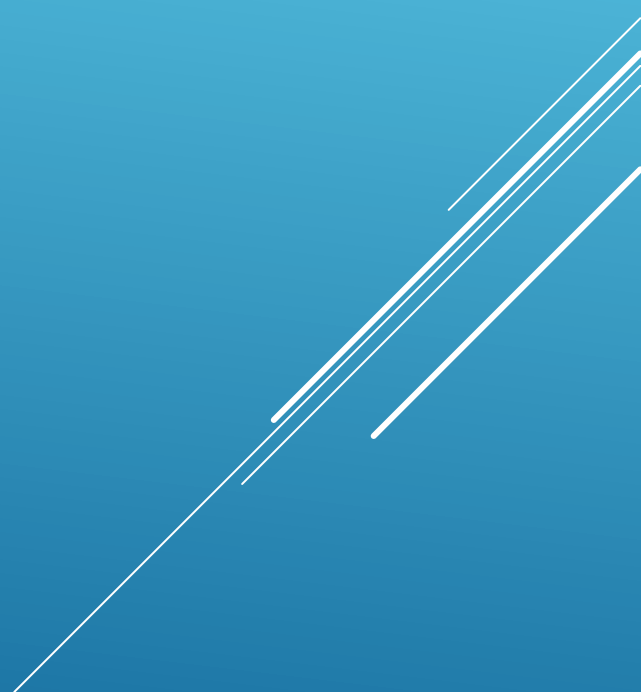Several thin, parallel white lines are drawn diagonally across the bottom right corner of the slide, extending from the right edge towards the center.

IN THE FUTURE

If we developed it further, it could be used in real fire-alarm systems, smart home safety devices, or automatic emergency-response systems.

Several thin, white, parallel lines of varying lengths and orientations are positioned in the bottom right corner of the slide, creating a modern, abstract graphic element.

CONCLUSION

This project is a simple and effective demonstration of temperature detection using basic electronic components.

The circuit works as a practical heat alarm or temperature-triggered switch.

